

NAVODAYA INSTITUTE OF TECHNOLOGY, RAICHUR

DEPARMENT OF COMPUTER SCIENCE & ENGINEERING

IOT Lab

Program - 05

05 Develop a program to deploy smart street light system using LDR sensor.

Components Required

- Arduino Uno (or similar board)
- 1 × LDR (Light Dependent Resistor)
- 1×10 k Ω resistor (for LDR voltage divider)
- $1 \times \text{LED}$ (for demo) + 220 Ω resistor, or Relay Module + AC bulb for real street light
- Breadboard + jumper wires

Working Principle

- The LDR's resistance changes with light:
 - o Bright light → Low resistance → Higher voltage at analog pin
 - o Dark → High resistance → Lower voltage at analog pin
- Arduino reads this voltage via **analog pin (A0)**.
- If value < threshold (dark), the street light (LED/relay) turns ON.
- If value > threshold (bright), the street light turns OFF.

Circuit Connections

- 1. LDR + Resistor Voltage Divider
 - \circ One side of LDR \rightarrow 5V
 - Other side of LDR \rightarrow **A0** and one side of 10kΩ resistor
 - \circ Other side of resistor \rightarrow GND
- 2. Street Light (Demo with LED)
 - o Arduino D7 → LED (through 220Ω resistor) → GND

 \bigcirc For real-world: Replace LED with a **relay module IN pin** at D7 \rightarrow relay controls AC bulb.

Steps to Do the Experiment

- 1. Connect the circuit as above.
- 2. Open Arduino IDE \rightarrow paste code (below).
- 3. Upload program to Arduino.
- 4. Open **Serial Monitor** (9600 baud) to observe LDR readings.
- 5. Cover the LDR \rightarrow LED/Street light turns ON.
- 6. Shine light on LDR \rightarrow LED turns OFF.
- 7. Adjust **threshold value** in code after checking readings.

Arduino Program

```
// Smart Street Light using LDR and Arduino
```

```
int LDR_Pin = A0; // LDR connected to A0
int Light_Pin = 7; // LED/Relay connected to D7
int LDR_Value = 0;
int Threshold = 500; // Adjust after testing your LDR readings
void setup() {
pinMode(Light_Pin, OUTPUT);
Serial.begin(9600);
void loop() {
 LDR_Value = analogRead(LDR_Pin); // Read LDR value
 Serial.print("LDR Value: ");
 Serial.println(LDR_Value);
 if (LDR_Value < Threshold) {
  digitalWrite(Light_Pin, HIGH); // Turn ON light (dark condition)
  Serial.println("Street Light ON");
  digitalWrite(Light_Pin, LOW); // Turn OFF light (bright condition)
  Serial.println("Street Light OFF");
 delay(500);
}\
```