



NAVODAYA INSTITUTE OF TECHNOLOGY, RAICHUR

DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING

IOT Lab Program - 04

04 Develop a program to control a DC motor with Arduino board

Components Required

- Arduino Uno (or any compatible board)
 - 1 × DC motor
 - 1 × Motor driver IC/module (L293D, L298N, or an H-bridge module — **never connect motor directly to Arduino pin**)
 - External power supply for motor (e.g., 6V or 9V battery pack, depending on motor rating)
 - Breadboard + jumper wires
-

✂ Why use a motor driver?

Arduino pins can supply **only ~40mA current**, while motors need much more.

A driver like **L293D / L298N** acts as an interface, allowing Arduino to safely control direction and speed.

Circuit Connections (Example: L293D driver IC)

Motor connections

- Motor → L293D pin 3 (OUT1) and pin 6 (OUT2)

Control signals from Arduino

- Arduino D8 → L293D pin 2 (IN1)
- Arduino D9 → L293D pin 7 (IN2)
- Arduino D10 (PWM) → L293D pin 1 (Enable1, ENA)

Power

- L293D pin 16 → 5V (logic supply)
 - L293D pin 8 → External motor supply (e.g., 6–12V, depending on motor)
 - All grounds (Arduino GND, L293D GND, motor power GND) → common
-

Logic of the Program

1. **ENA (Enable)** controls motor **speed** using `analogWrite()` (PWM).
 2. **IN1 / IN2** decide **direction**:
 - IN1 = HIGH, IN2 = LOW → Motor forward
 - IN1 = LOW, IN2 = HIGH → Motor reverse
 - Both LOW → Motor stop
-

Arduino Program (DC Motor with L293D)

```
// Pin definitions
int ENA = 10; // PWM pin for speed control
int IN1 = 8; // Motor driver input 1
int IN2 = 9; // Motor driver input 2

void setup() {
  pinMode(ENA, OUTPUT);
  pinMode(IN1, OUTPUT);
  pinMode(IN2, OUTPUT);
}

void loop() {
  // Motor Forward
  digitalWrite(IN1, HIGH);
  digitalWrite(IN2, LOW);
  analogWrite(ENA, 200); // Speed (0-255)
  delay(3000);

  // Stop
  digitalWrite(IN1, LOW);
  digitalWrite(IN2, LOW);
  delay(2000);

  // Motor Reverse
  digitalWrite(IN1, LOW);
  digitalWrite(IN2, HIGH);
  analogWrite(ENA, 150); // Lower speed
  delay(3000);

  // Stop
  digitalWrite(IN1, LOW);
  digitalWrite(IN2, LOW);
  delay(2000);
}
```

Steps to Perform the Experiment

1. Connect the **motor, driver IC, and Arduino** as described.
2. Upload the sketch from Arduino IDE.
3. Observe the motor:
 - Runs **forward** at speed ~200 PWM for 3 seconds.
 - Stops for 2 seconds.
 - Runs **reverse** at speed ~150 PWM for 3 seconds.
 - Stops again.
4. Repeat in loop.
5. Try changing the `analogWrite(ENA, value)` (0–255) to control speed.