



# NAVODAYA INSTITUTE OF TECHNOLOGY, RAICHUR

## DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING

### IOT Lab

### Program - 02

---

## 02 Develop a program to interface a relay with Arduino board

### 1. Components Required

- Arduino Uno (or any Arduino board)
- 1 × Relay Module (5V relay, single-channel)
- 1 × Load (like a small AC bulb or DC motor, for demo you can use an LED with external power supply)
- Jumper wires
- Breadboard

⚠ **Safety Note:** If you connect an AC appliance, take extreme care — never touch wires when powered. For beginners, test with a DC bulb or motor first.

---

### 2. Circuit Connections

If using a **ready-made relay module** (recommended):

- **Relay IN pin** → Arduino Digital Pin 7
- **Relay VCC** → 5V (Arduino)
- **Relay GND** → GND (Arduino)
- **Relay Output (COM, NO, NC terminals)** → Connect external load.
  - COM = Common (input supply for load, e.g., +V of external power)
  - NO (Normally Open) = Load connects when relay is activated.
  - NC (Normally Closed) = Load connects when relay is off.

🔗 Example: Connect a **5V bulb** between **NO** and **GND of external supply**, and supply +5V to COM.

---

### 3. Logic of the Program

- Set relay pin as **OUTPUT**.
- Write **HIGH** to energize the relay (turn ON load).
- Write **LOW** to de-energize the relay (turn OFF load).
- Add a delay to toggle repeatedly.

---

#### 4. Arduino Program (C++)

```
int relayPin=7; // Relay module connected to digital pin 7

void setup() {
  pinMode(relayPin, OUTPUT); // Set relay pin as output
}

void loop() {
  digitalWrite(relayPin, HIGH); // Turn relay ON
  delay(2000);                // Wait 2 seconds

  digitalWrite(relayPin, LOW); // Turn relay OFF
  delay(2000);                // Wait 2 seconds
}
```

---

#### 5. Upload & Test

- Upload the sketch to Arduino.
- The relay will **click ON and OFF every 2 seconds**.
- Your connected device (LED bulb/fan/motor) will turn ON and OFF accordingly.